

Name _____

Electrical Circuits Parallel and Series Batteries Activity Sheet

Materials:	1 - #40 bulb	8 - 15 cm copper wires	4 batteries	1 switch
	1 – bulb holder	4 battery holders	1 screwdriver	

Circuit A on page 13 of SAB

1. Construct Circuit A. Close the switch and observe.

Are the batteries connected in series or parallel? _____

How can you prove this? _____

2. Predict what will happen to the brightness of the bulb if two more batteries are added to Circuit A in series.

Add two more batteries in series to Circuit A. What do you observe about the bulb?

Circuit B on page 13 of SAB

3. Construct Circuit B. Note the polarity of the batteries. Close the switch and observe.

Are the batteries connected in series or parallel? _____

How can you prove this? _____

Electrical Circuits Parallel and Series Batteries Activity Sheet (cont.)

4. Predict what will happen to the brightness of the bulb if two more batteries are added in parallel to Circuit B.

Add two more batteries in parallel to Circuit B. What do you observe?

5. What is the **voltage** of one battery? _____

6. When batteries are connected in **series**, the voltage of all batteries is added together.

How much voltage is in a series circuit with four batteries? _____

How much voltage is in a series circuit with seven batteries? _____

7. When batteries are connected in **parallel**, the voltage is the same as one battery.

How much voltage is in a parallel circuit with four batteries? _____

How much voltage is in a parallel circuit with seven batteries? _____

8. You are taking a battery powered nightlight with you camping. Would you want the batteries wired in series or parallel? Explain your answer.
